

HW #5. Simple Buffer Insertion

(Due: 5/31/2017)

In this program, you need to insert buffers in front of nodes to reduce delay time.

1. Goal:

- (1) Read a wire resistance and node capacitance sequences of a non-fork (one-line) circuit and a buffer library.
- (2) Add buffers in front of nodes to make **delay** < **max allowed delay**.
- (3) Your solution should **minimize the cost** and **cannot violate the max allowed delay**. (The cost and delay calculation are mentioned in Section 3.)
- (4) If the costs of valid insertion combination are the same, please output the one with minimal delay.

2. Input and Output Format:

2.1 Input file: input.txt

```
testcase_num
max_allowed_delay           //case1


node_num                    //Circuit Information
1  $\Omega_1$   $C_1$ 
2  $\Omega_2$   $C_2$ 
3  $\Omega_3$   $C_3$ 
...

buf_num                     //Buffer Library
1  $\Omega_{buf1}$   $C_{buf1}$   $Cost_{buf1}$ 
2  $\Omega_{buf2}$   $C_{buf2}$   $Cost_{buf2}$ 
...                          //case 2.....
```

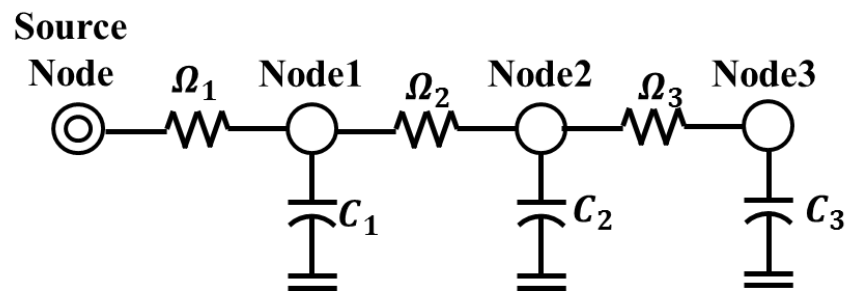(1) Circuit Information

First line is the number of nodes. Then, each line includes node_id, the resistance of wire i (Ω_i) and the capacitance of node i (C_i).

The circuit consists of those nodes in order. (Source node -> node 1 -> node 2 -> node 3 ...)



(2) Buffer Library

First line is the number of kinds of buffers in buffer library. Each line contains buffer_id, the resistance of buffer k ($\Omega_{buf\ k}$), the capacitance of buffer k ($C_{buf\ k}$) and the cost of buffer k ($Cost_{buf\ k}$).

You need to choose which kind of buffer to insert. Each kind of buffer can be chosen repeatedly.

2.2 Output file: output.txt

One case is showed in one line, and different cases are splited by newline.

(1) Solvable

You should list insertion position (node_id) and inserted buffer_id in one line, splited by space and sorted by node_id.

e.g. Insert buffer 2 on node 1 and buffer 1 on node 3

1 2 3 1 //node_id buf_id node_id buf_id ...

(2) No Solution

If there is no valid combination of inserting buffers to make delay < max_allowed_delay, you should write “NO SOLUTION” in output.txt.

e.g.

NO SOLUTION

3. Relative Formula

3.1 Cost Calculation

$$cost = \sum_{\text{buffer } k \text{ you insert}} Cost_{bufk}$$

e.g. if you insert buffer 1 on node 1 and buffer 2 on node 3, your cost is $Cost_{buf1} + Cost_{buf2}$.


3.2 Delay Calculation

The delay from source node to last node is shown below:

$$delay = \sum_{\text{node } i \in \text{circuit}} \Omega_i * dscap_i$$

$dscap_i$ is the downstream capacitance which means accumulated capacitance from last node to node i.

(1) Without buffers

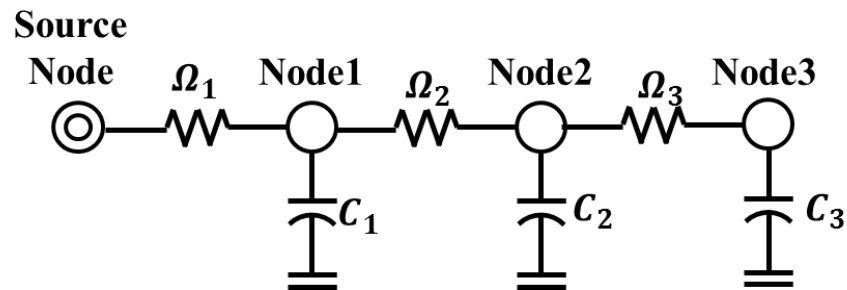


$$\begin{aligned} \text{delay} = & \Omega_1 * (C_1 + C_2 + C_3) + \\ & \Omega_2 * (C_2 + C_3) + \\ & \Omega_3 * C_3 \end{aligned}$$

(2) Insert buffers

If you insert a buffer k on node i, the $dscap_i$ will be replaced by the capacitance of inserted buffer (C_{bufk}). But the delay should plus $\Omega_{bufk} * \text{original } dscap_i$.


e.g.

a) Insert buffer 1 on node 3

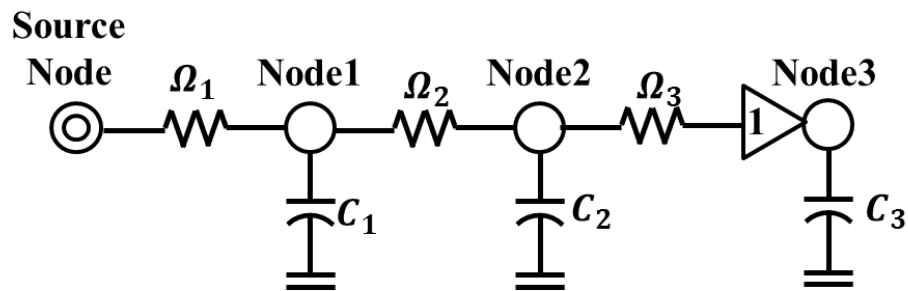

$$\begin{aligned} \text{delay} = & \Omega_1 * (C_1 + C_2 + C_{buf1}) + \\ & \Omega_2 * (C_2 + C_{buf1}) + \\ & \Omega_3 * C_{buf1} + \\ & \Omega_{buf1} * C_3 \end{aligned}$$

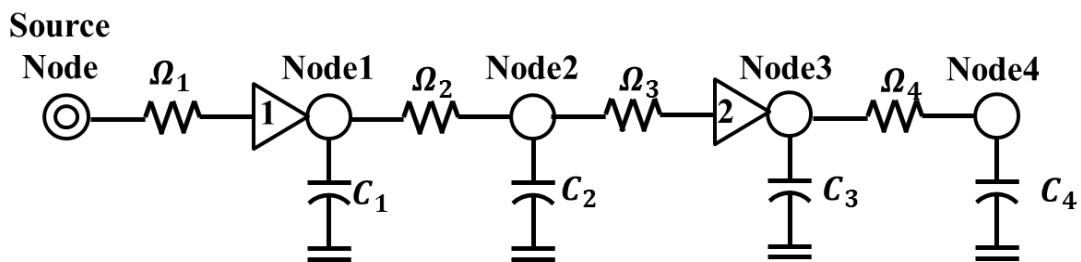b) Insert buffer 1 on node 1 and buffer 2 on node 3



$$\begin{aligned} \text{delay} = & \Omega_1 * C_{buf1} + \\ & \Omega_{buf1} * (C_1 + C_2 + C_{buf2}) + \\ & \Omega_2 * (C_2 + C_{buf2}) + \\ & \Omega_3 * C_{buf2} + \\ & \Omega_{buf2} * (C_3 + C_4) + \\ & \Omega_4 * C_4 \end{aligned}$$

3.3 Verify

We provide a “Verify” program to show delay and cost of your solution.

- Usage: ./Verify [input_filename] [output_filename]
- If it cannot be executed, use the following command:
\$ chmod +x Verify

4. Example

input.txt

```
2 // 2 cases
2000 // case 1

3
1 44 10.61
2 10 20
3 10 15

2
1 6.12 3.5 11.5
2 44 0.42 1.03

500 // case 2

3
1 44 10.61
2 10 20
3 10 15

2
1 6.12 3.5 11.5
2 44 0.42 1.03
```

output.txt

```
1 1 // case 1 result
NO SOLUTION // case 2 result
```

\$./Verify input.txt output.txt

[vrf] Case 1

Node 3

Delay: 150

Dscap: 15

Cost: 0

Node 2

Delay: 500

```

        Dscap: 35
        Cost: 0
Node 1
        Delay: 933.133
        Dscap: 3.5
        Cost: 11.5
===== solution info =====
Delay: 933.133
Slack: 1066.87           //Slack = Max_Allowed_Delay - Delay
Cost: 11.5
-----
-----
[vrf] Case 2
NO SOLUTION
Node 3
        Delay: 150
        Dscap: 15
        Cost: 0
Node 2
        Delay: 500
        Dscap: 35
        Cost: 0
Node 1
        Delay: 2506.84
        Dscap: 45.61
        Cost: 0
===== solution info =====
Delay: 2506.84
Slack: -2006.84          //Slack = Max_Allowed_Delay - Delay
Cost: 0
-----

```

5. Discussion Board

If you have any problem about this homework, please post your question in our [discussion board](#). You are encouraged to post the question on discussion board as others might have the similar question.